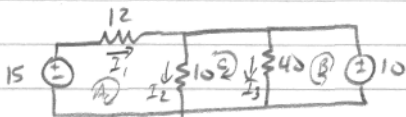


HW #1 SOLN

1.



$$I_1 = I_A$$

$$I_2 = I_A - I_C$$

$$I_3 = I_B + I_C$$

$$15 = 22I_A - 10I_C$$

$$10 = 40I_B + 40I_C$$

$$0 = 50I_C - 10I_A + 40I_B$$

$$\begin{pmatrix} 15 \\ 10 \\ 0 \end{pmatrix} = \begin{pmatrix} 22 & 0 & -10 \\ 0 & 40 & 40 \\ -10 & 40 & 50 \end{pmatrix} \begin{pmatrix} I_A \\ I_B \\ I_C \end{pmatrix}$$

$$I_A = .416$$

$$I_B = .833$$

$$I_C = -.583$$


$$I_1 = 0.416 \text{ A}$$

$$I_2 = 1 \text{ A}$$

$$I_3 = 0.25 \text{ A}$$

2. SAME CIRCUIT BY SUPERPOSITION

A) 10V short

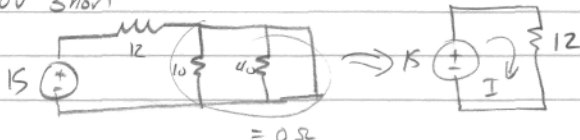


$$I_{12} = \frac{15}{12} \text{ A} = 1.25 \text{ A} \rightarrow$$

$$I_{10} = 0$$

$$I_{40} = 0$$

B) 15V short

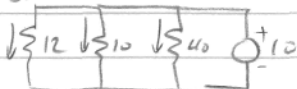

$$I_{40} = \frac{10V}{40} = .25 \text{ A} \downarrow$$

$$I_{10} = \frac{10}{10} = 1 \text{ A} \downarrow$$

$$I_{12} = \frac{10V}{12\Omega} = .833 \leftarrow$$


$$\text{TOTAL: } I_1 = 1.25 \text{ A} - .833 = .417 \text{ A}$$

$$I_2 = 1 \text{ A}$$

$$I_3 = .25 \text{ A}$$

AGREES

3.

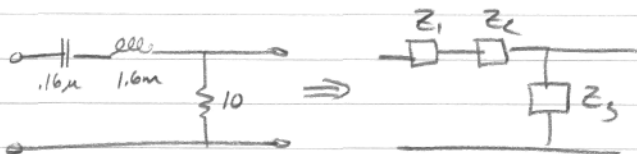

$$\frac{V_0}{V_1} = \frac{Z_3}{Z_1 + Z_2 + Z_3} = \left(\frac{R}{R + j\omega L - \frac{j}{\omega C}} \right) \frac{\omega C}{\omega C}$$

$$= \frac{\omega R C}{R\omega C + j(\omega^2 LC - 1)}$$

$$\left| \frac{V_0}{V_1} \right| = \frac{\omega R C}{[(\omega R C)^2 + (\omega^2 LC - 1)^2]^{1/2}}$$

Resonance @ $\omega^2 LC = 1$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Turn to software to "look" at freq response.


If $R_L = 10\Omega$ (same value of R)

$$\frac{V_0}{V_1} = \frac{Z_3}{Z_1 + Z_2 + Z_3 + Z_4} = \frac{R}{2R + j\omega L - \frac{j}{\omega C}}$$

ONLY change is $R \rightarrow 2R$ in denominator

$$C := 0.16 \cdot 10^{-6} \quad L := 1.6 \cdot 10^{-3} \quad R := 10$$

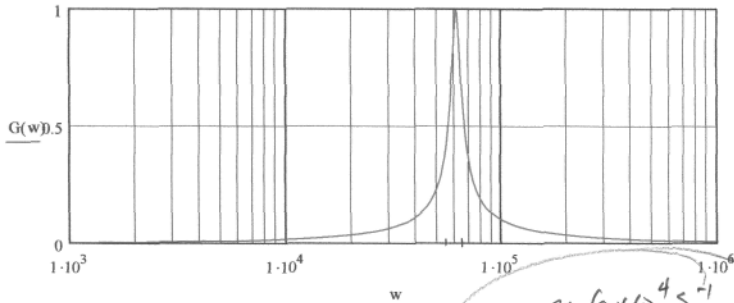
$$G(w) := \frac{w \cdot R \cdot C}{\sqrt{(w \cdot R \cdot C)^2 + (w^2 \cdot L \cdot C - 1)^2}} \quad w := 100, 1000 \dots 10000000$$



$$\omega_0 \sim 6 \times 10^4 \text{ s}^{-1}$$

With Added Internal Resistance of Inductor = 10Ω $BW \sim 1 \times 10^4 \text{ s}^{-1}$


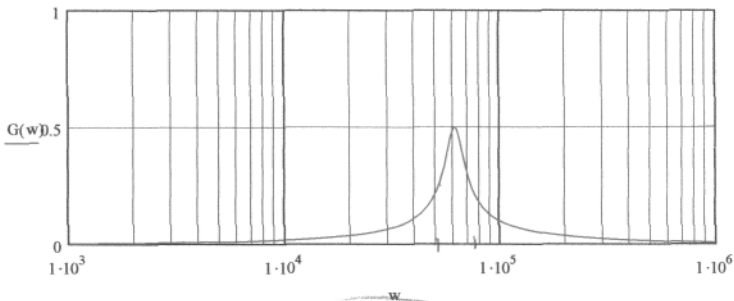
$$G(w) := \frac{w \cdot R \cdot C}{\sqrt{(w \cdot 2R \cdot C)^2 + (w^2 \cdot L \cdot C - 1)^2}}$$



$$\omega_0 \approx 6 \times 10^4 \text{ s}^{-1}$$

$$BW \sim 2.5 \times 10^4 \text{ s}^{-1}$$

4.

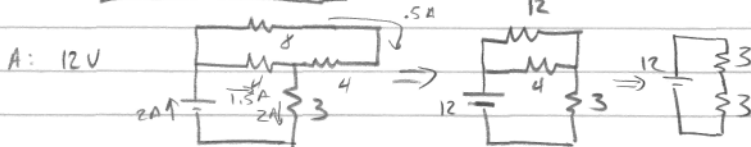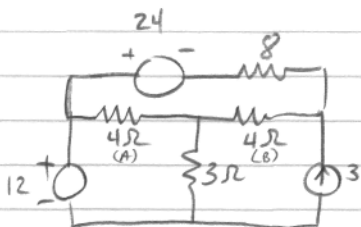

$$I = \frac{12V}{6\Omega} = 2A$$


This means 2A out of 12V & 2A thru 3Ω.

There is therefore 6V difference across 4Ω (A)

∴ 4Ω + 8Ω P.H. For 4Ω (A), $I_{4A} = \frac{6V}{4\Omega} = 1.5A$

4 + 8Ω (B) $I = \frac{6V}{12} = 0.5A$

B. 24V

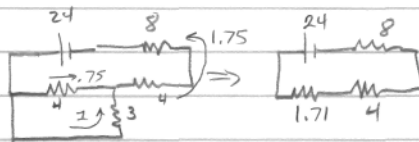

$$I = \frac{24V}{13.71} = 1.75A$$



→ 1.75A Thru 24V, 8Ω & 4Ω (B)

→ 3V across 4Ω || 3Ω

results in " 1A thru 3Ω "

.75A thru 4Ω

C. 3A

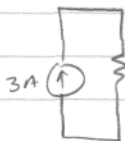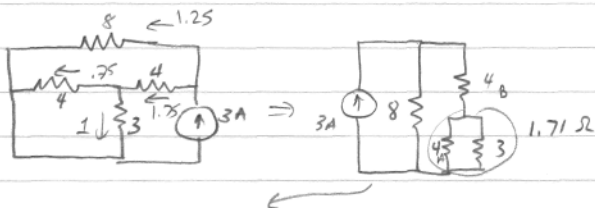

$$\Rightarrow V = 10V$$

$$\therefore I_8 = \frac{10V}{8} = 1.25A$$

$$I_{4B} = 1.75A$$

$$V_{4||3} = (1.71A)(3\Omega) = 5.13V$$

$$\therefore I_{4A} = .75A$$

$$I_{3A} = 1A$$

The question is what is I thru 3Ω Resistor.
Three contributions are:

$$\left. \begin{array}{l} 12V: 2A \downarrow \\ 24V: 1A \uparrow \\ 3A: 1A \downarrow \end{array} \right\} 2A \uparrow$$