

CHEMISTRY 133
Additional Problem 1.2.5

In one type of hygrometer, water vapor pressure affects the capacitance reading. Given the following circuit with a 0.00 V to 5.00 V square wave in, estimate C if the output wave looks as follows.

