

CHEMISTRY 133
Spring, 2015 Homework Set 1
Only Problems in Bold are Submitted for Grading

Set 1.1 - Complete for quiz on Feb. 5


Statistics Calculations (See Chem. 133 Lab Manual pages 3-4):

- 1. Download the file on the Chem 133 website labeled HW11.txt. (this gives the time in minutes and the signal in fluorescence units) and transfer to an Excel File. Print a table from Excel showing two columns collected over the first 30 s period.**
- 2. Make a plot of the raw data from above and also data processed with a 2 s moving average over both the first 30 s. This can be done by either using Excel's Plotting routines or by creating a 2 s moving average using a new column in Excel.**
- 3. Given the following data, determine the concentration of levoglucosan in an unknown and the standard deviation in its concentration.**


Calibration Data..... Unknown Data

Levoglucosan conc (ug/mL)	Levoglucosan Area	Levoglucosan conc (ug/mL)	Levoglucosan Area
0.5	469.11	Unknown	2276.40
1	826.57		
2	1578.66		
5	3973.85		
10	8043.47		

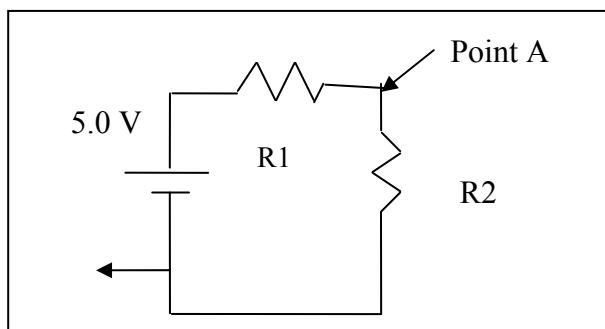
4. In the circuit to the right, with $R_1 = 250 \Omega$, $R_2 = 1250 \Omega$, calculate:
 - a) the voltage at point A (relative to ground).
 - b) the current through point A
 - c) the power dissipated in both resistors



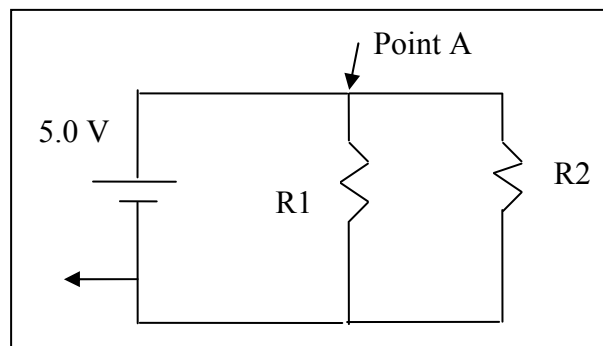
5. Given the following circuit to the right with $R_1 = 500 \Omega$, and $R_2 = 1000 \Omega$, determine:
 - a) the current through each resistor.
 - b) the power dissipated in each resistor.



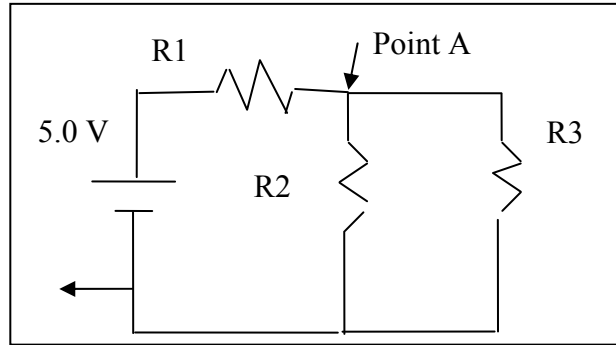
6. In the following circuit to the right with R_1 , R_2 , and R_3 equal to 120, 240 and 180 Ω , respectively, calculate the voltage at point A and the current through R_3 .



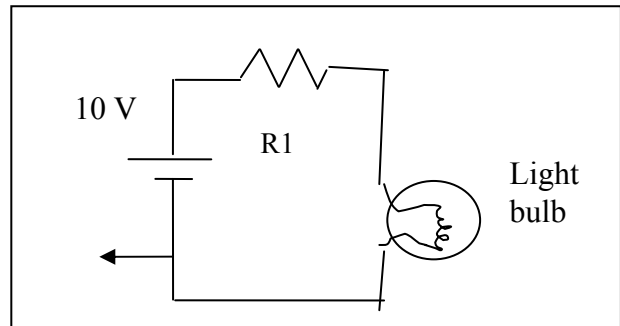7. Calculate the resistance of R_1 in order to have 15 W of power supplied to the light bulb if the resistance of the light bulb is 3.4 Ω .



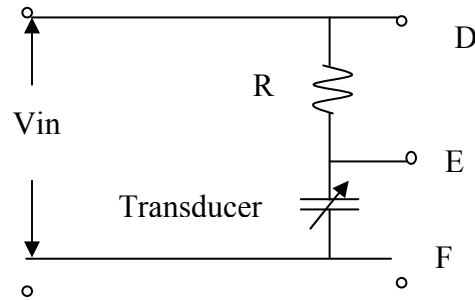8. Some hygrometers, instruments that measure water vapor, contain a capacitor with a material that absorbs water between the metal plates. As the water vapor pressure increases, the capacitance increases. At time $t = 0$ in the circuit to the right, V_{in} changes instantaneously from -2.00 V to +2.00 V. Given that the resistance value of the resistor is 32.0 k Ω ,




- If the voltage between points E and F is +0.50 V at $t = 0.100$ s, calculate the capacitance of the transducer.
- What would be the voltage between points D and E at $t = 0.100$ s?
- What would be the voltage between points E and F at $t = 0.42$ s?


Additional Problems:

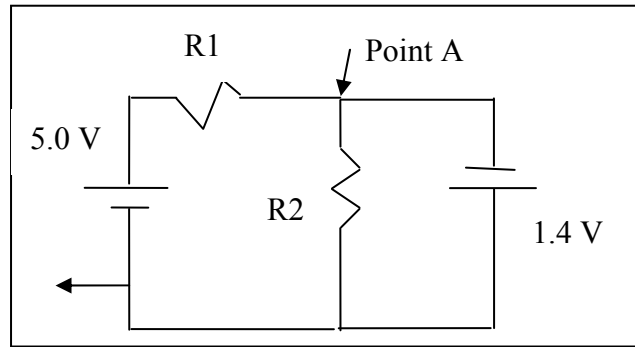1. Given the following circuit to the right with $R_1 = 360 \Omega$ and $R_2 = 140 \Omega$ determine:

- the current through each resistor.
- the voltage at point A.
- the power dissipated through R_2 .



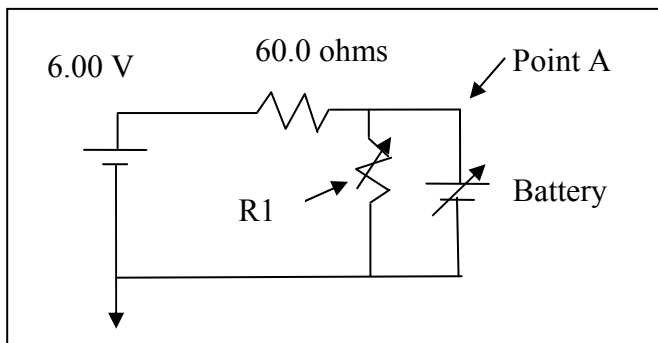2. The following circuit can be use to charge a battery.



The battery is initially at 1.71 V, but a fully charged battery should have a charge of 2.50 V.

- Determine the initial Voltage at point A (note that this is independent of R_1)
- It is important not to allow too much current to the battery when charging (as this decreases battery lifetime). What resistance at R_1 should be used to limit the current to the battery to 50 mA?
- As the battery is charged and reaches 2.50 V, what is the new current (assuming R_1 doesn't change)?

3. In the circuit to the right, at $t = 0$, V_{in} changes from -3.00 V to 0.00 V. $R = 285 \text{ k}\Omega$ and $C = 3.0 \times 10^{-6} \text{ F}$.

- What is the current (in μA) flowing from D and E at $t = 0.40 \text{ s}$?
- At what time will the voltage between E and F reach -1.00 V?

