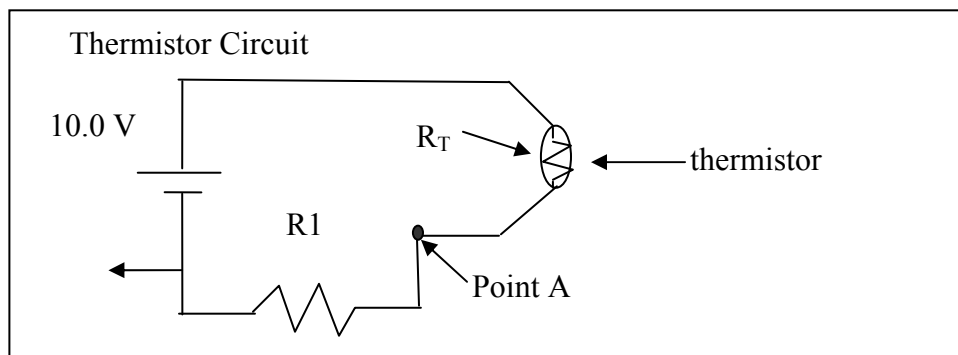


CHEMISTRY 133
Quiz 1 – 10 points
SOLUTIONS

The circuit below is set up to measure temperature using a thermistor. The thermistor is a resistor in which the resistance, R_T , varies with temperature. In the circuit below with $R_1 = 521 \Omega$, if the voltage at point A is 3.96 V,

a) Calculate R_T .

b) Thermistors often give erroneous readings due to self-heating (the measured temperature is hotter than the true temperature because of resistive heating). What is the power dissipated in the thermistor?



a) across resistor, R_1 , $V = V_A - 0 = 3.96 \text{ V} = IR_1$ or $I = 3.96 \text{ V} / 521 \Omega = 0.00760 \text{ A}$

across thermistor, $V = 10 - V_A = 10.0 \text{ V} - 3.96 \text{ V} = 6.04 \text{ V} = IR_T$ or $R_T = 6.04 \text{ V} / 0.00760 \text{ A} = 795 \Omega = \mathbf{790 \Omega}$ (2 sig figs)

b) $P = IV = (0.00760 \text{ A})(6.04 \text{ V}) = \mathbf{0.046 \text{ W}}$