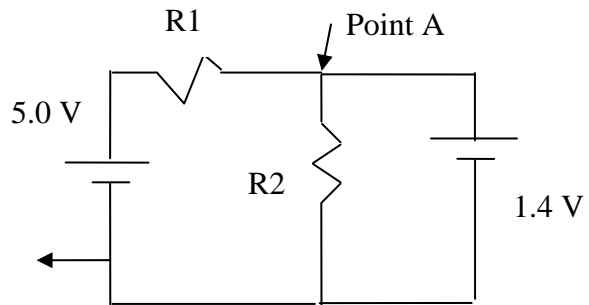


Set 1.1 – Additional Problems


1.1.1. Given the following circuit to the right with $R_1 = 360 \Omega$ and $R_2 = 140 \Omega$

determine:


- a) the current through each resistor.**
- b) the voltage at point A.**
- c) the power dissipated through R_2 .**



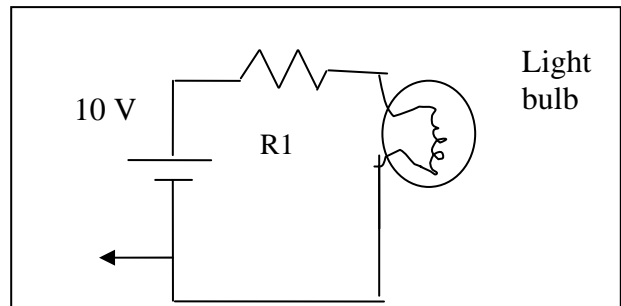1.1.2. Calculate the resistance of R_1 in order to have 15 W of power supplied to the light bulb if the resistance of the light bulb is 3.4Ω .



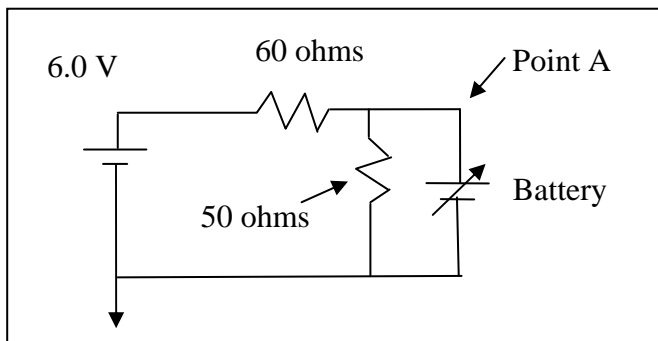1.1.3. The following circuit can be use to charge a battery.



- a) If the battery initially can supply a potential (or voltage) of 2.3 V, calculate:**
 - i) the potential at point A (relative to ground)**
 - ii) the current through the 60 ohm resistor (defined from +6.0 V to Point A)**
 - iii) the current to the battery (from top to bottom)**
- b) As the battery is charged (and its potential increases), what is the voltage it will reach where it no longer receives current from the 6.0 V power supply?**