CPE/EEE 64 PAL Worksheet

DECODERS AND ENCODERS WORKSHEET

1) A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2ⁿ unique output lines. If the n -bit coded information has unused combinations, then what happens to the decoder output?

Example 1) Using a decoder and external gates, design the combinational circuit defined by the following Boolean functions,

$$F_1 = x'yz' + xz$$


$$F_2 = xy'z' + x'y$$

$$F_3 = x'y'z' + xy$$

$$F_{1} = x'yz' + xz(y + y') = x'yz' + xyz + xy'z = \sum (2,5,7)$$

$$F_{2} = xy'z' + x'y(z + z') = xy'z' + x'yz + x'yz' = \sum (2,3,4)$$
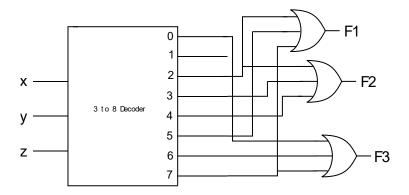
$$F_{3} = x'y'z' + xy(z + z') = x'y'z' + xyz + xyz' = \sum (0,6,7)$$



2)

Using a decoder and external gates, design the combinational circuit defined by the following Boolean functions,

$$F_1 = (y' + z)x$$

$$F_2 = y'z' + x'y + yz'$$

$$F_3 = (x + y)z$$


Example 2) How many 2x4 decoders will be required to implement 4x16 decoder?

$$16/4 = 4$$

$$4/4 = 1$$


- 3) How many 3x8 decoders will be required to implement 6x64 decoder?
- 4) How many 4x16 decoders will be required to implement 8x256 decoder?

CPE/EEE 64 PAL Worksheet

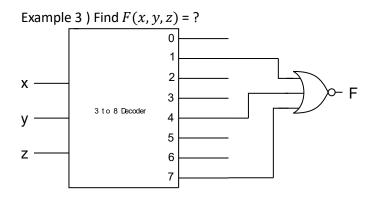

Since a NOR gate connected to output $F(x, y, z) = \sum (0.2, 3.5, 6)$

5) Find F(x, y, z) = ?

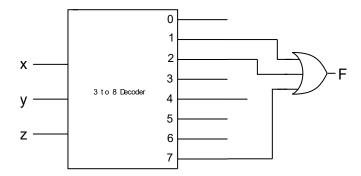

An encoder has 2n (or fewer) input lines and n output lines. The output lines, as an aggregate, generate the binary code corresponding to the input value.

- 6) A decimal to binary encoder will have how many inputs and outputs?
- 7) The output 2-bit comparator is logic 1 when the input X is greater than the input Y. How do you calculate the total number of combinations for which the output is logic 1?
- 8) Explain if and how a BCD to seven segment conversion requires an encoder or decoder.
- 9) Can an encoder can be built by using which basic logic gate? Explain how.
- 10) Can a decoder be built by using which universal gate? Shown an example.