
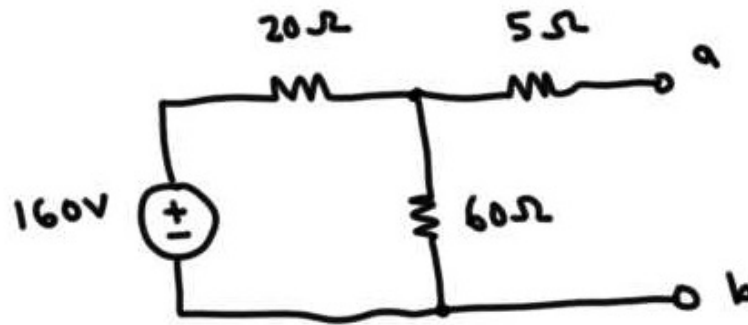


Thevenin Equivalent Circuits: Given a linear network, it is always possible to replace the network with a voltage source in series with a resistor.

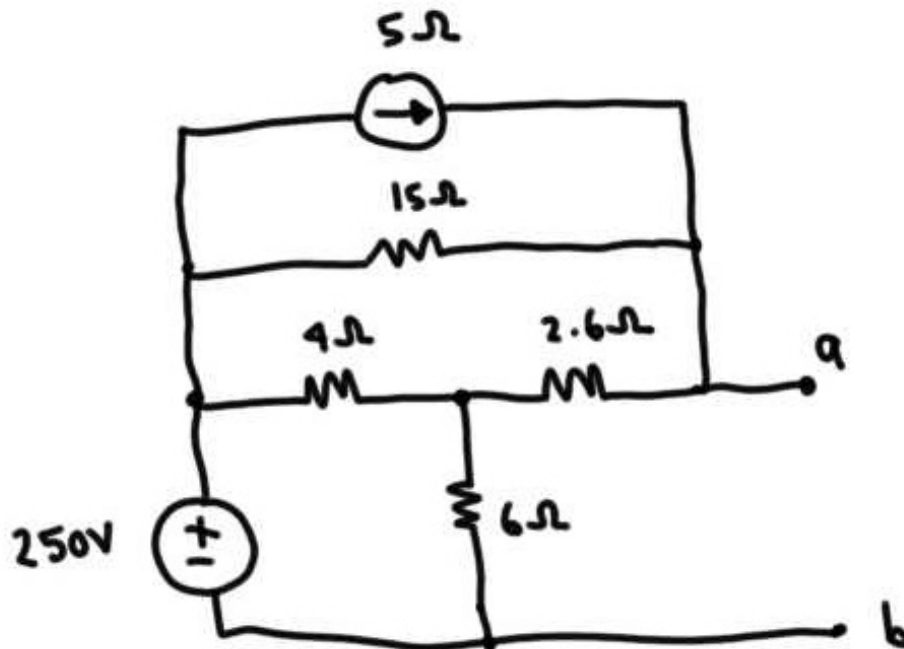- 1) Find the Thevenin equivalent with respect to terminals a,b in the circuit shown below by finding the following:
 - a) Find the open circuit voltage, V_{oc} , with respect to the terminals a, b.
 - b) Find the short circuit current, i_{sc} , with respect to the terminals a, b.
 - c) Calculate the Thevenin resistance, R_{Th} , and sketch the Thevenin equivalent circuit with respect to the terminals a, b.




- 2) Find the Thevenin equivalent with respect to terminals a,b in the circuit shown below. Sketch the Thevenin equivalent circuit showing all the relevant calculated values.




Norton Equivalent Circuits: Given a linear network, it is always possible to replace the network with a current source in parallel with a resistor.

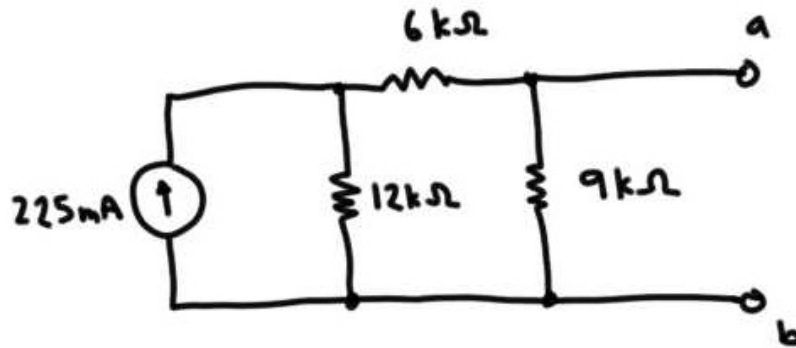- 1) Find the Norton equivalent with respect to terminals a,b in the circuit shown below by finding the following:
 - a) Find the open circuit voltage, V_{oc} , with respect to the terminals a, b.
 - b) Find the short circuit current, i_{sc} , with respect to the terminals a, b.
 - c) Calculate the Thevenin resistance, R_{Th} , and sketch the Norton equivalent circuit with respect to the terminals a, b.




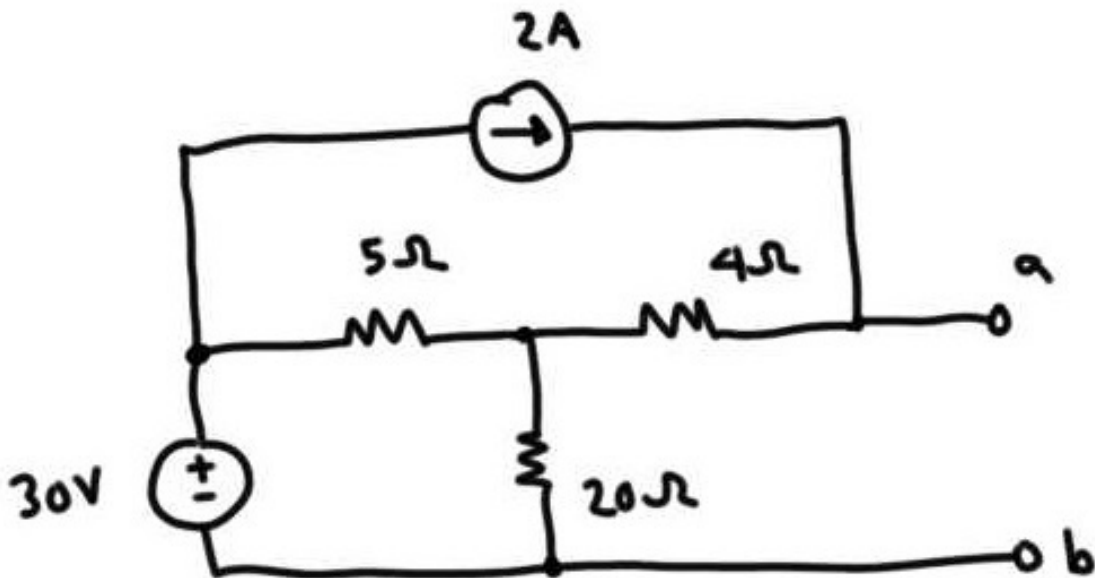- 2) Find the Norton equivalent with respect to terminals a,b in the circuit shown below. Sketch the Norton equivalent circuit showing all the relevant calculated values.



Special Cases: Sometimes finding the Thevenin or Norton equivalent circuits is not as straight forward. Here are some interesting and challenging cases where finding the equivalents is possible yet requires a bit more insight and thought.

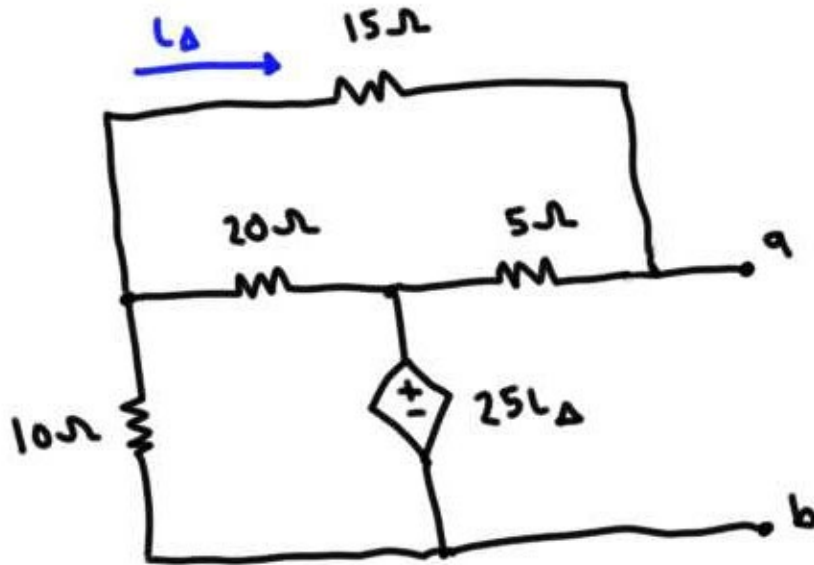- 1) Find the Thevenin equivalent with respect to terminals a, b.



- 2) Find the Norton equivalent with respect to terminals a, b.

