
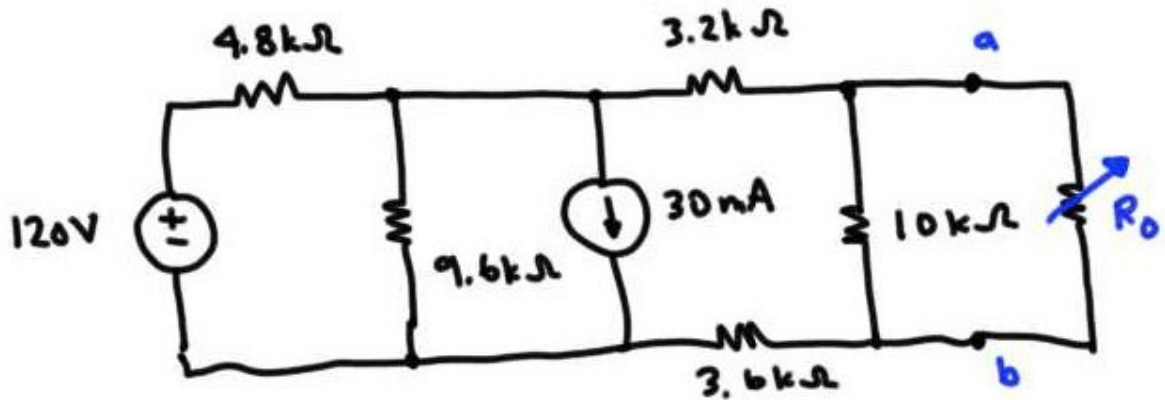


**Maximum Power Transfer:** Given a linear network, the maximum power is delivered to a load resistor only if the load resistance matches the Thevenin resistance of the linear network.

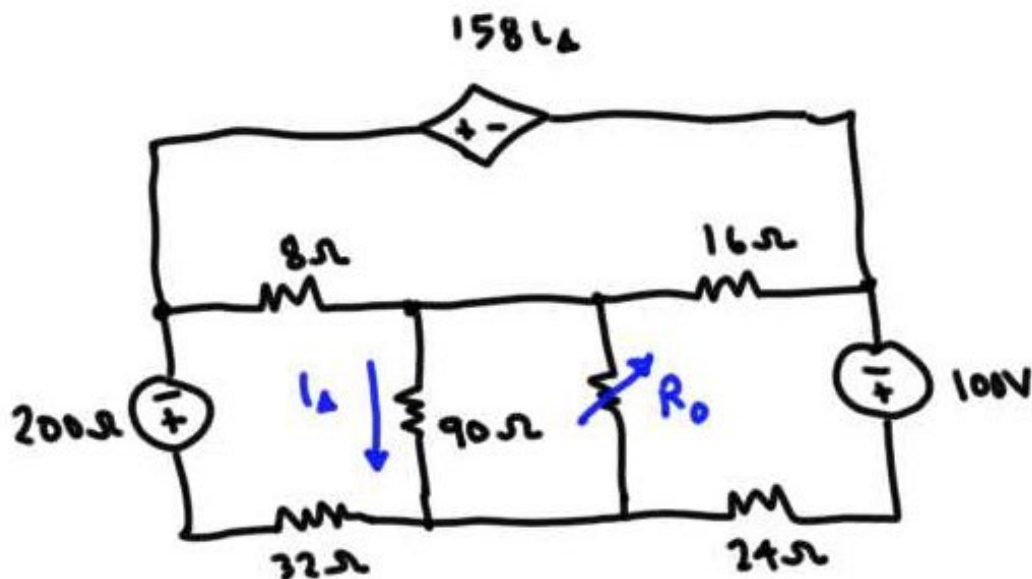- 1) The variable resistor is adjusted for maximum power transfer to  $R_0$ .




- a) Find the value of  $R_0$ .
  - b) Find the maximum power that can be delivered to  $R_0$ .
- 2) The variable resistor has been adjusted until it absorbs the maximum power from the circuit shown below.
    - a) Find the value of  $R_0$ .
    - b) Find the maximum power that can be delivered to  $R_0$ .



**Superposition:** Given a linear network, any circuit voltage or current can be calculated as the algebraic sum of the individual voltages or currents caused by each independent source acting alone.

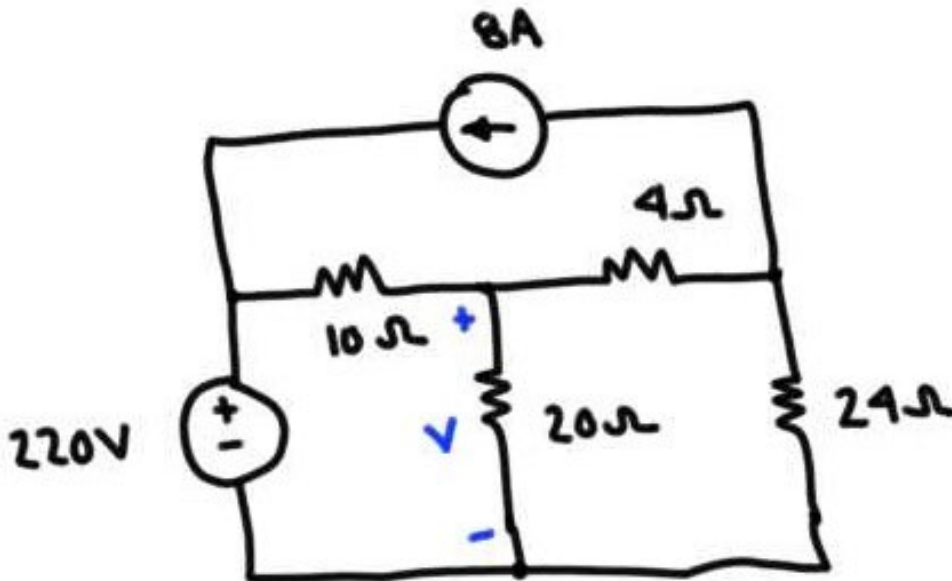- 1) Use the principle of superposition to find the voltage  $v_0$  in the circuit. Also find the power dissipated in the  $20\Omega$  resistor.



- 2) Use superposition to find  $v_0$  and  $i_0$  in the circuit shown below.

