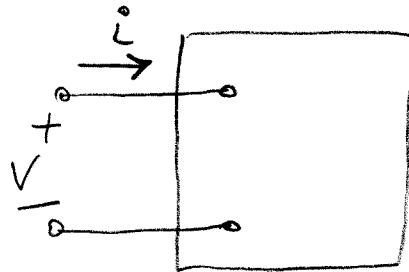


Chapter 1 - circuit Variables

Passive sign convention



$$\text{Power} = \frac{dw}{dt} = v i$$

$$P > 0$$

Power absorbed
by the circuit

$$P < 0$$

Power delivered
by the circuit

Chapter 2 - Circuit Elements

 Ideal Voltage Source - maintains voltage regardless of current in the device.
(true)

 Ideal Current Source - maintains current regardless of the voltage across the device.

 Dependent Sources - value determined by some other source

Ohm's Law $V = iR$

$$P = v i = i^2 R = \frac{V^2}{R}$$

Node - 2 or more circuit elements join

Kirchoff's current law $\sum_{\text{node}} i = 0$ at any node

Kirchoff's voltage law $\sum_{\text{loop}} v = 0$ around any closed path



Chapter 3 - Simple Resistive Circuits

"Resistors add in Series"

$$R_{eq} = R_1 + R_2 + \dots + R_k$$

Parallel Req


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Two resistors in parallel


Voltage Divider

$$V_1 = \frac{R_1}{R_1 + R_2} V_S$$

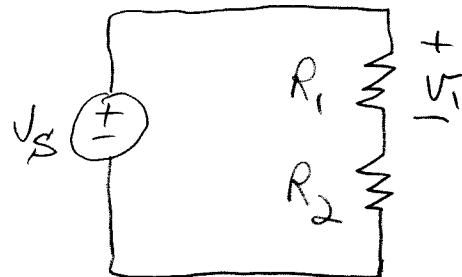


Current Divider


$$i_1 = \frac{R_2}{R_1 + R_2} i_S$$

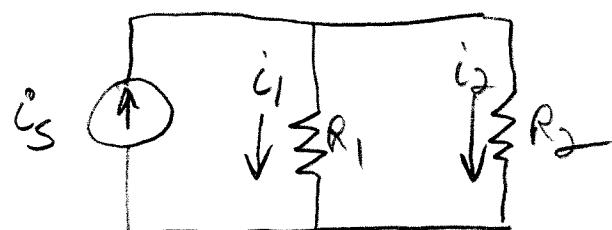

Delta to Wye (or Pi to Tee)

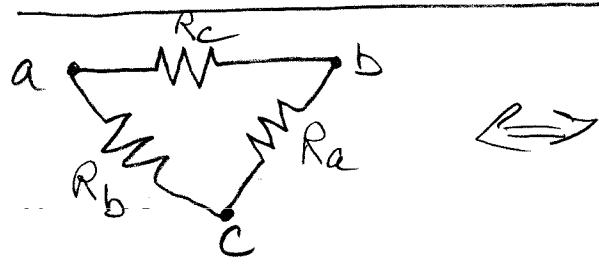

Be able to solve transform
a if given the eqns.

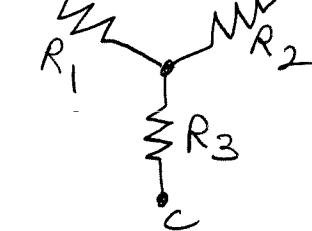


Chap 4 - Techniques of Circuit Analysis

Knows how to apply the definitions of node, essential node, path, branch, essential branch, and mesh

Node-Voltage - choose reference node & write current in/out of the node in terms of the voltage variables ($\frac{V_1 - V_2}{R}$)


Mesh-Current → assign reference currents in a loop. Write the sum of the voltages (current × resistance) around the loop = zero.

Source Transform

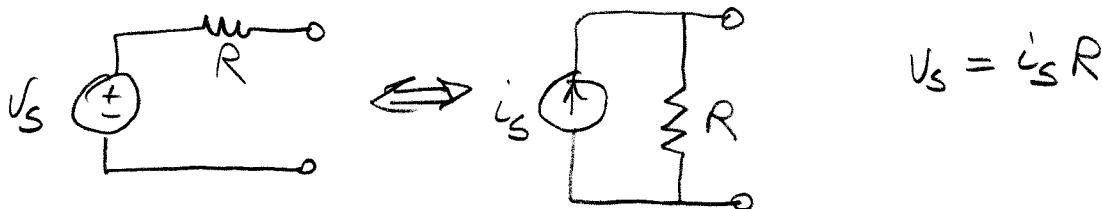


Thevenin Equivalent - simplify circuit to
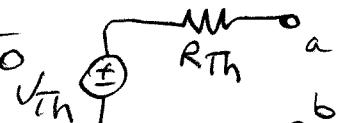
$$V_{Th} = V_{\text{open circuit}} \text{ (at terminal ab)}$$



Norton Equivalent - simplify to
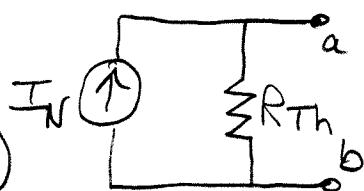
$$I_N = I_{\text{short circuit}} \text{ (across terminal ab)}$$



$$R_{Th} = \frac{V_{Th}}{I_{SC}}$$

We possible (usually simpler) find R_{Th} by deactivating the Independent sources & then apply series or parallel combinations to find R_{eq}


When Dependent Sources are in the circuit - you must apply a "test" voltage V_T , find current I_T (by circuit analysis)

$$R_{Th} = \frac{V_T}{I_T}$$

The trick is to restate the dependent source in terms of V_T & I_T .

max Power

max when $R_{Load} = R_{Th}$.

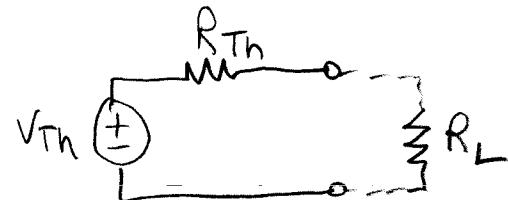

$$P = \frac{V_{Th}^2}{4 R_L}$$


Superposition → for a linear system, you can find the result (v or i) for each independent source individually & then sum all the results into the complete answer.

All equations marked with * will be given to you on the test

Chapter 5 - Ideal Op-Amp

Sec 5.1 thru 5.4

(5.6 & 5.7 not covered)

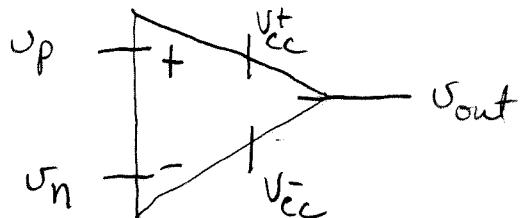

V_{out} must be \leq supply voltage

$$V_o = \begin{cases} -V_{cc} \\ A(V_p - V_n) \\ +V_{cc} \end{cases}$$

$$V_p = V_n$$

$$i_p = i_n = 0$$

Be able to use node-voltage analysis to solve for

$$V_{out} = k V_{in} \quad \text{where } k = \text{scaling factor}$$

$$\text{Inverting Amplifier} \quad V_o = -\frac{R_f}{R_s} V_{in}$$

$$\text{Summing Amplifier} \quad V_o = -\left(\frac{R_f}{R_a} V_a + \frac{R_f}{R_b} V_b + \frac{R_f}{R_c} V_c\right)$$

$$\text{non-inverting Amplifier} \quad V_o = \frac{R_s + R_f}{R_s} V_{in}$$

Examine the circuits in the chapter

2

Chapter 6 - Sec 6.1 thru 6.3
 (Sec 6.4 & 6.5 not covered)

Inductance - relates induced voltage (induced by a time varying magnetic field) to the current.

Capacitance - relates displacement current (produced by a time-varying electric field) to the voltage.

Inductor

$$v = L \frac{di}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v \, dt + i(t_0)$$

$$\text{power } p = L i \frac{di}{dt}$$

$$\text{energy } w = \frac{1}{2} L i^2$$

Inductors add in series

$$L_{\text{eq}} = L_1 + L_2 + \dots + L_n \text{ (series)}$$

$$\frac{1}{L_{\text{eq}}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n} \text{ (parallel)}$$

Capacitor

$$v = \frac{1}{C} \int_{t_0}^t i \, dt + v(0)$$

$$i = C \frac{dv}{dt}$$

$$*p = C v \frac{dv}{dt}$$

$$w = \frac{1}{2} C v^2$$

Capacitors add in parallel

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \text{ (series)}$$

$$C_{\text{eq}} = C_1 + C_2 + \dots + C_n \text{ (parallel)}$$

Chapter 7 - Response of 1st order RL and RC circuits

Natural Response - no source but can have initial energy.

Step Response - sudden onset of constant voltage or current.

RL circuit (Natural Response)

$$i(t) = I_0 e^{-\frac{R}{L}t} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{for } t \geq 0$$

$$v(t) = I_0 R e^{-\frac{R}{L}t} \quad \left. \begin{array}{l} \\ \end{array} \right\} \tau = \frac{L}{R}$$

$$P_{\text{power}} = vi = i^2 R = \frac{v^2}{R} = I_0^2 R e^{-2\frac{t}{\tau}} \quad t \geq 0^+$$

$$* \text{energy } W = \frac{1}{2} L I_0^2 (1 - e^{-2\frac{t}{\tau}}) \quad t \geq 0$$

Steady state \triangleq 5 time constants

RC circuit (Natural Response)

$$v(t) = V_0 e^{-\frac{t}{\tau}} \quad t \geq 0 \quad \tau = RC$$

$$i(t) = \frac{V_0}{R} e^{-\frac{t}{\tau}} \quad t \geq 0^+ \quad V_0 = \text{initial capacitor voltage}$$

$$* P = \frac{V_0^2}{R} e^{-2\frac{t}{\tau}} \quad t \geq 0^+$$

$$* W = \frac{1}{2} C V_0^2 (1 - e^{-2\frac{t}{\tau}}) \quad t \geq 0$$

RL circuit (Step Response)

$$\left. \begin{aligned} \text{* } i(t) &= \frac{U_s}{R} + \left(I_0 - \frac{U_s}{R} \right) e^{-\frac{t}{T}} \\ \text{* } v(t) &= (U_s - I_0 R) e^{-\frac{t}{T}} \end{aligned} \right\} \quad t \geq 0$$

recall $V_L = L \frac{di}{dt}$
so derivative involved
in $v(t)$)

RC circuit (Step Response)

$$\left. \begin{aligned} \text{* } v_c(t) &= I_s R + (V_0 - I_s R) e^{-\frac{t}{T}} \\ \text{* } i_c(t) &= (I_s - \frac{V_0}{R}) e^{-\frac{t}{T}} \end{aligned} \right\} \quad t \geq 0 \quad i = c \frac{dv}{dt}$$

again derivative involved

general soln (sec 7.4) not on the test.
sequential switching (sec 7.5) not on the test

sec 7.6 Unbounded Response

must have dependent source!

$R_{Th} \rightarrow$ negative resistance (Thévenin resistance)

usually use "test method" to find

$$\frac{v_T}{i_T} = R_{Th}$$

(Hint: remember Thévenin + Norton equivalents is one of the three things you learn in this course!)

Sec 7.7 Integrating Op-Amp

see fig 7. 40 on page 316

$$\star v_o(t) = \frac{-1}{R_s C_f} \int_{t_0}^t v_s d\tau + v_o(t_0)$$

Chapter 8 N.R. & S.R. for RLC circuits - 2nd order system

characteristic eqn. $s^2 + 2\zeta s + \omega_0^2 = 0$

$$\text{roots } s_{1,2} = -\zeta \pm \sqrt{\zeta^2 - \omega_0^2}$$

$$\begin{aligned} \zeta &= \frac{1}{2RC} \text{ (Parallel)} \\ &= \frac{R}{2L} \text{ (series)} \end{aligned} \quad \left. \right\} \text{Nepel Frequency}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{resonant radian frequency}$$

overdamped $\omega_0^2 < \zeta^2$ (or $\zeta^2 > \omega_0^2$)

$s_{1,2} = \text{real \& distinct roots}$

Sluggish response

underdamped $\omega_0^2 > \zeta^2$

$s_{1,2} = \text{complex conjugate pair roots } (x \pm jy)$

rapid but "ringing" response - decaying oscillations

critically damped $\omega^2 = \omega_0^2$

$s_{1,2} = \text{real + repeating roots}$
 "on the verge" of oscillating

Natural Response

$$\text{over } *x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$*x(0) = A_1 + A_2$$

$$*\frac{dx(0)}{dt} = s_1 A_1 + s_2 A_2$$

$$\text{under } *x(t) = (B_1 \cos \omega_d t + B_2 \sin \omega_d t) e^{-\alpha t}$$

$$*x(0) = B_1$$

$$*\frac{dx(0)}{dt} = -\alpha B_1 + \omega_d B_2$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

Critical

$$*x(t) = (D_1 t + D_2) e^{-\alpha t}$$

$$*x(0) = D_2$$

$$*\frac{dx(0)}{dt} = D_1 - \alpha D_2$$

solve for voltage (or current) at once then find
 the current (or voltage).

Step Response

over $* x(t) = x_{final} + A_1' e^{s_1 t} + A_2' e^{s_2 t}$

$$* x(0) = x_f + A_1' + A_2'$$

$$* \frac{dx(0)}{dt} = A_1' s_1 + A_2' s_2$$

under

$$* x(t) = x_f + (B_1' \cos \omega_d t + B_2' \sin \omega_d t) e^{-\alpha t}$$

$$* x(0) = x_f + B_1'$$

$$* \frac{dx(0)}{dt} = -\alpha B_1' + \omega_d B_2'$$

critical

$$* x(t) = x_f + D_1' t e^{-\alpha t} + D_2' e^{-\alpha t}$$

$$* x(0) = x_f + D_2'$$

$$* \frac{dx(0)}{dt} = D_1' - \alpha D_2'$$

Know how to use these equations!

Also, clearly relate V_{cap} to $I_{inductor}$ for all times but in particular at $t=0$ and $t=\infty$

Chapter 9 - Sinusoidal steady-state Analysis

$$v(t) = V_m \cos(\omega t + \theta)$$


$$\omega = 2\pi f = \frac{2\pi}{T} \text{ rad/sec}$$

$$\theta^\circ \left(\frac{\pi}{180^\circ} \right) = (\text{radians/sec})$$

$$V_{rms} = \sqrt{\underbrace{\frac{1}{T} \int_{t_0}^{t_0+T} \underbrace{V_m^2 \cos^2(\omega t + \theta)}_{\text{square}} dt}_{\text{mean over one period } T}}$$

(square) root

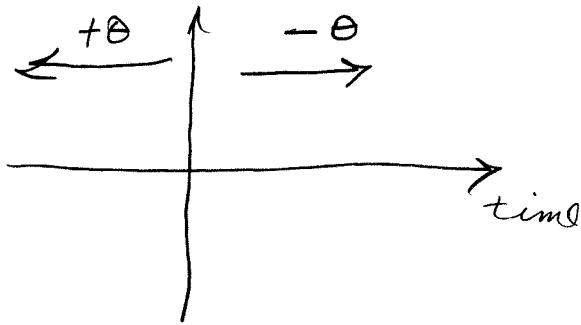for cos or sin $V_{rms} = \frac{V_m}{\sqrt{2}}$



$$\sin(\theta) = \cos(\theta - 90^\circ)$$

Total Response = Transient + steady state

steady state solution for linear systems

① response is a sinusoidal

② freq remains the same.

③ all else may vary.

Resistor $\nabla = IR$ no phase shift

Inductor $v = L \frac{di}{dt}$ "current lags the voltage"

$$\nabla = j\omega L I$$

Capacitor $i = c \frac{dv}{dt}$

$$\nabla = j\left(\frac{1}{\omega c}\right) I$$
 "current leads the voltage"

Impedance

$$\nabla = z I$$

$$z = \begin{cases} R & \text{resistor} \\ j\omega L & \text{inductor} \\ j\left(\frac{1}{\omega c}\right) & \text{capacitor} \end{cases}$$

KVL & KCL all still apply - must now solve the complex number math.

Series

$$Z_{eq} = z_1 + z_2 + \dots + z_K$$



Parallel

$$\frac{1}{Z_{eq}} = \frac{1}{z_1} + \frac{1}{z_2} + \dots + \frac{1}{z_K} \quad Z_{eq} = \frac{z_1 z_2}{z_1 + z_2}$$

Δ to γ in freq domain \rightarrow not on the final

Thevenin & Norton

replace R_{Th} with Z_{Th}

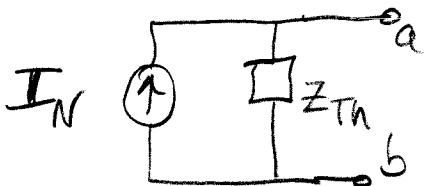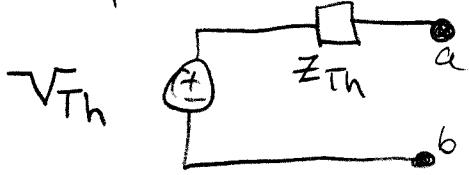

Node-voltage & mesh as before

Be sure to solve the complex number math carefully.

Chap 10 - Sinusoidal Steady-state Power

after the trig identities we write the power as

$$P_{\text{Total}} = P + P \cos 2\omega t - Q \sin 2\omega t$$

$$\text{where } P = \text{average power} = \frac{V_m I_m}{2} \cos(\theta_v - \theta_i)$$

$$Q = \text{reactive power} = \frac{V_m I_m}{2} \sin(\theta_v - \theta_i)$$

$$\text{note } \frac{V_m}{\sqrt{2}} = V_{\text{rms}} \stackrel{d}{=} V_{\text{eff}}$$

$$\frac{I_m}{\sqrt{2}} = I_{\text{rms}} \stackrel{d}{=} I_{\text{eff}}$$

$$P_f = \cos(\theta_v - \theta_i) \quad \text{power factor}$$

must state whether current is "leading" or "lagging".
(cap) (inductor)

$$R_f = \sin(\theta_v - \theta_i) \quad \text{reactive factor}$$

Complex Power

$$S = \text{apparent power} = P + j Q$$

$$= \frac{1}{2} V I^* = V_{rms} I_{rms}^*$$

$$= I_{rms}^2 (Z) = \frac{V_{rms}^2}{Z^*}$$

not a phasor

$$|S| = \sqrt{P^2 + Q^2} \quad \text{in units of Volt.Amp}$$

P has units of watt

Q has units of Volt.Amp.Reactive (VAR)

Max Power

$$Z_L = Z_{T_h}^* \quad P_{max} = \frac{1}{4} \frac{|V_{T_h}|^2}{R_L} = \frac{1}{8} \frac{V_m^2}{R_L}$$