


EIT Review

The following pages are the examples used in the DC Circuits review lecture presented at CSU Sacramento on behalf of the students and Tau Beta Pi honor society.

Questions and corrections should be addressed to
Russ Tatro
rtatro@csus.edu

Example

Power delivered to a resistor

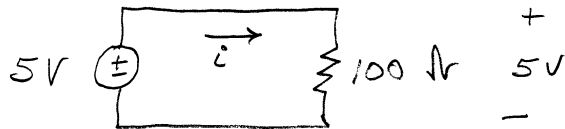

$$\begin{aligned} P_{100\Omega} &= (+) v i = i^2 R = \frac{v^2}{R} \\ &= \frac{(5V)^2}{100\Omega} = \frac{1}{4} \text{ Watt Absorbed} \end{aligned}$$


$$P_{5V \text{ source}} = (-) v i$$

$$\begin{aligned} i &= \frac{v}{R} = \frac{5V}{100\Omega} = \frac{1}{20} A = 0.05 A \\ &= 50 \text{ mA} \end{aligned}$$

$$= (-)(5V)(50 \text{ mA})$$

$$= -0.25 \text{ Watt delivered}$$

- KCL/KVL Example find i_0

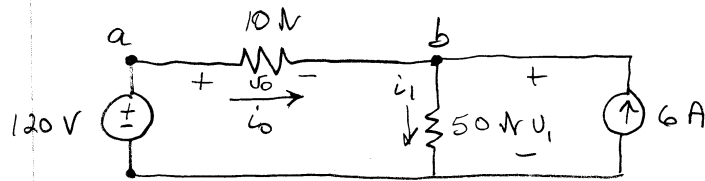

at node b: KCL

$\left. \begin{array}{l} \text{in} = - \\ \text{out} = + \end{array} \right\} \text{just be consistent!}$

$$\begin{aligned} -i_0 + i_1 - 6A &= 0 \\ i_1 &= i_0 + 6A \end{aligned}$$

Now use KVL around left loop

$$-120V + v_0 + v_1 = 0 \quad \text{where } v_0 = i_0 (10\Omega)$$

$$\begin{aligned} \text{so} \\ v_0 + v_1 &= 120V \\ v_1 &= (i_0 + 6A)(50\Omega) \end{aligned}$$


$$i_0 (10\Omega) + (i_0 + 6A)(50\Omega) = 120V$$

$$i_0 (60\Omega) = 120V - 300V = -180V$$

$$i_0 = -3A$$

the (-) sign means current is in the opposite direction from that initially drawn.

Series Resistance

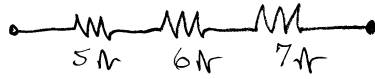

$$R_{\text{eq}} = 5 + 6 + 7 \\ = \underline{\underline{18 \Omega}}$$

Parallel Resistance




$$\frac{1}{R_{\text{eq}}} = \frac{1}{10} + \frac{1}{20} = \frac{2}{20} + \frac{1}{20} \\ = \frac{3}{20}$$

$$R_{\text{eq}} = \frac{20}{3} = \underline{\underline{6.67 \Omega}}$$

$$\text{or } R_{\text{eq}} = \frac{10 \cdot 20}{10 + 20} = \frac{200}{30} = \underline{\underline{6.67 \Omega}}$$


Voltage Divider

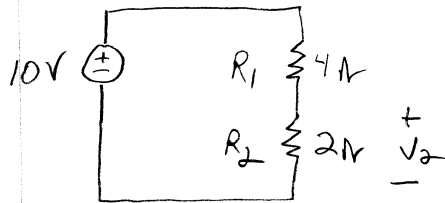

$$\begin{aligned} \text{find } V_2 \quad V_2 &= \frac{R_2}{R_1 + R_2} V \\ &= \frac{2 \Omega}{4 \Omega + 2 \Omega} (10 \text{ V}) \\ &= \frac{2}{6} (10 \text{ V}) = \underline{\underline{3.33 \text{ V}}} \end{aligned}$$

Current Divider

find i_2

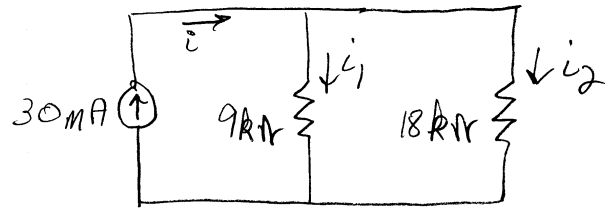


$$i_2 = \frac{R_1}{R_1 + R_2} i$$

$$= \frac{9 \text{ k}\Omega}{9 \text{ k}\Omega + 18 \text{ k}\Omega} (30 \text{ mA})$$

$$= \frac{9}{27} (30 \text{ mA}) = \frac{1}{3} (30 \text{ mA})$$

$$= \underline{\underline{10 \text{ mA}}}$$

Node Analysis

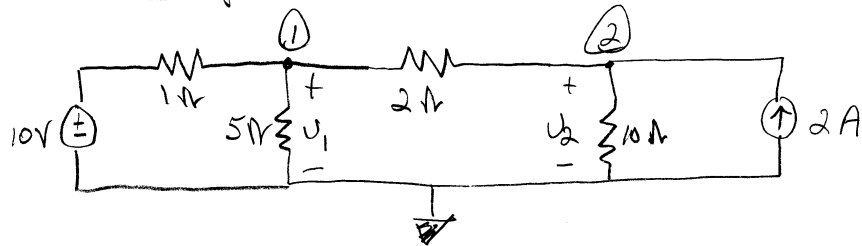

① Pick reference node - I picked the bottom

② Define the non-reference nodes

③ write the equations $\sum i = 0$

$$\text{node ①} \quad \frac{V_1 - 10V}{1\Omega} + \frac{V_1}{5\Omega} + \frac{V_1 - V_2}{2\Omega} = 0$$

$$\text{node ②} \quad \frac{V_2 - V_1}{2\Omega} + \frac{V_2}{10\Omega} + (-)2A = 0$$


put in "standard form" for your calculator

$$\text{node ①} \quad 10V_1 - 100V + 2V_1 + 5V_1 - 5V_2 = 0$$

$$V_1(17) + V_2(-5) = 100V$$

$$\text{node ②} \quad V_1(-5) + V_2(6) = 20A$$

mesh Analysis

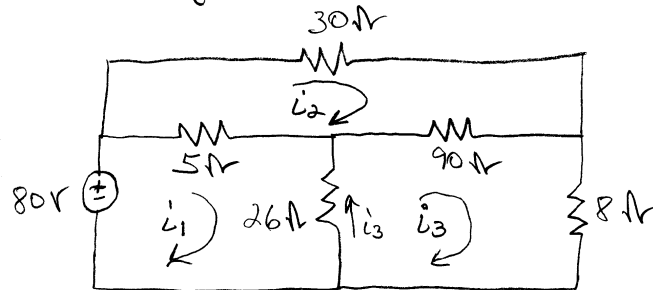

① Assign mesh currents

② write KVL around the loop

mesh i_1

$$-80V + (i_1 - i_2)5\Omega + (i_1 - i_3)26\Omega = 0$$

$$i_1(31\Omega) + i_2(-5\Omega) + i_3(-26\Omega) = 80V$$

mesh i_2

$$i_2(30\Omega) + (i_2 - i_3)90\Omega + (i_2 - i_1)5\Omega = 0$$

$$i_1(-5\Omega) + i_2(125\Omega) + i_3(-90\Omega) = 0$$


mesh i_3

$$(i_3 - i_2)90\Omega + i_3(8\Omega) + (i_3 - i_1)26\Omega = 0$$


$$i_1(-26\Omega) + i_2(-90\Omega) + i_3(124\Omega) = 0$$

Plug into calculator $i_1 = 5A$



Source Transformations

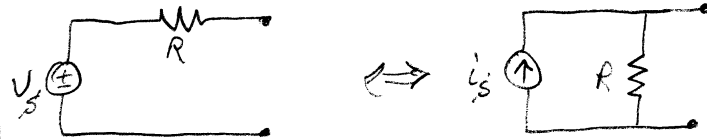
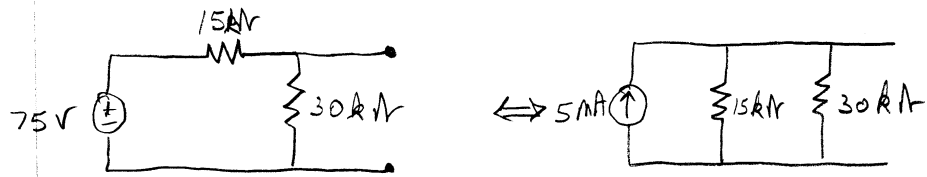
$$V_s = i_s R \quad \Leftrightarrow \quad i_s = \frac{V_s}{R}$$




$$i_s = \frac{75V}{15k\Omega} = 5mA$$

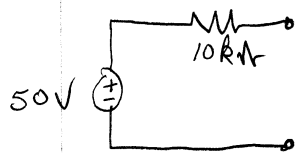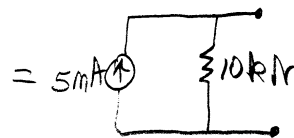


$$\begin{aligned} \Leftrightarrow V_s &= i_s R = (5mA)(10k\Omega) \\ &= 50V \end{aligned}$$


Norton

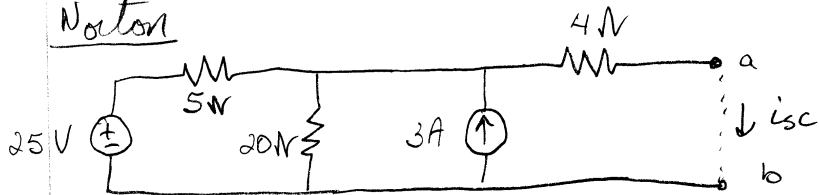

for I_N find i_{sc}

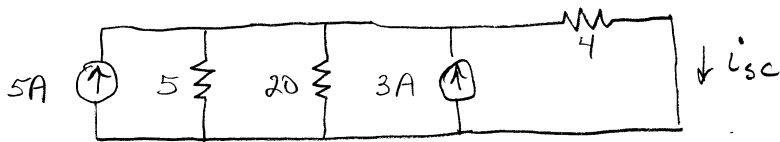


$$5 \parallel 20 = 4 \Omega$$

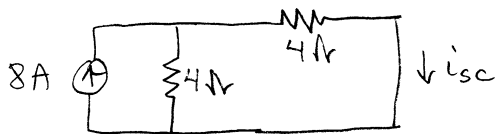

By logic $i_{sc} = 4A$ or by current divider

$$i_{sc} = \frac{4}{4+4} (8A) = \frac{1}{2} (8A) = 4A$$



we already found $R_{Th} = 8 \Omega$

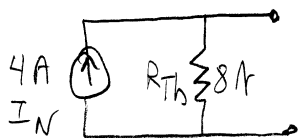

By confirmation

$$I_N = \frac{V_{Th}}{R_{Th}} = \frac{32V}{8\Omega} = 4A$$

Thevenin - Focus on terminal behavior

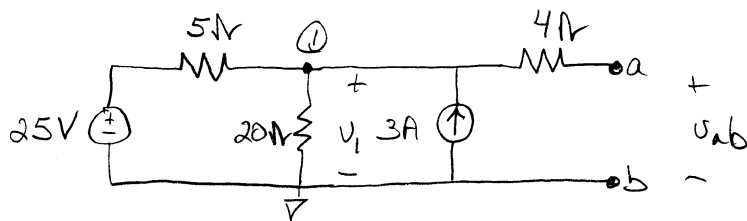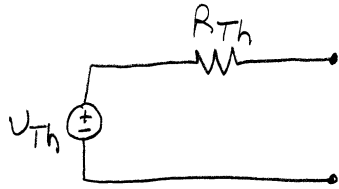



use node to find U_1 $U_1 = U_{Th}$!

$$\frac{U_1 - 25V}{5\Omega} + \frac{U_1}{20\Omega} - 3A = 0$$

$$4U_1 - 100V + U_1 - 60V = 0$$


$$5U_1 = 160V \Rightarrow U_1 = \underline{\underline{32V}} = U_{Th} \text{ for } U_{ab} = \text{open circuit}$$

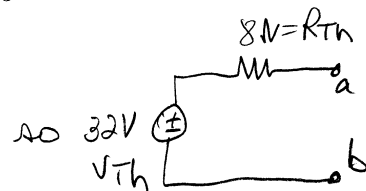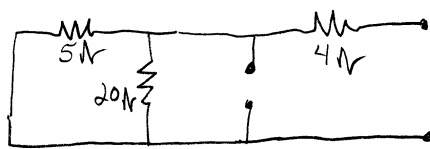Find R_{Th} → "kill the independent sources"



$$5 // 20 + 4 = 4 + 4 = 8\Omega$$


Max Power

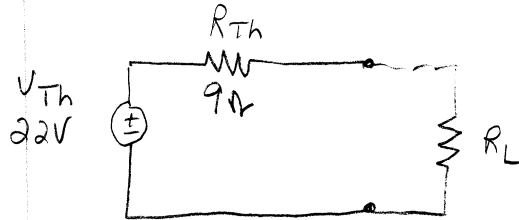

max power delivered when $R_L = R_{Th} = 9\ \Omega$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(22V)^2}{4(9\ \Omega)} = \frac{484}{36}\ \text{W}$$
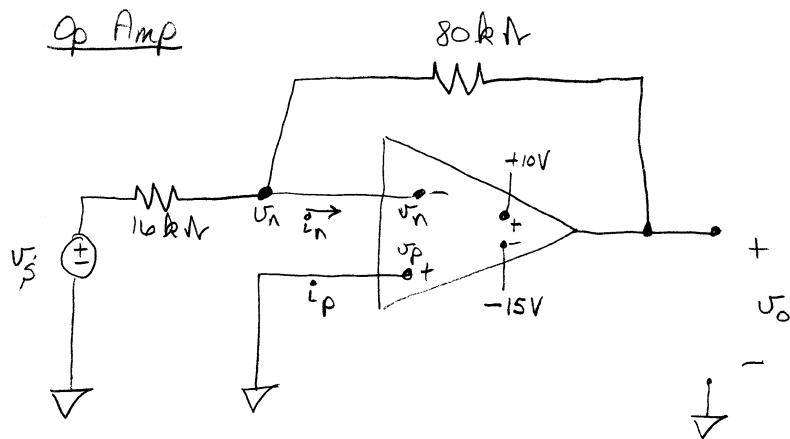
$$= \underline{\underline{13.44\ \text{watts}}}$$



By Ideal Op Amp $i_n = i_p = 0$

$U_n = U_p$ in this case $U_p = 0$

node eqn

$$\frac{U_n - U_s}{16 \text{ k}\Omega} + i_n + \frac{U_n - U_o}{80 \text{ k}\Omega} = 0 \quad \begin{array}{l} i_n = 0 \\ U_n = 0 \end{array}$$

$$\frac{-U_s}{16 \text{ k}\Omega} - \frac{U_o}{80 \text{ k}\Omega} = 0$$

$$U_o = (-) \frac{80 \text{ k}\Omega}{16 \text{ k}\Omega} U_s = \underline{\underline{(-5) U_s}}$$

Op Amp (2)

What is the range of v_o in the linear region?

$$-V_{CC} \leq A(v_p - v_n) \leq +V_{CC} \quad \text{where } (-5)v_o = A(v_p - v_n)$$

$$-15V \leq (-5)v_o \leq 10V \quad \text{mult by } -\frac{1}{5}$$

$$+3V \geq v_o \geq -2V$$

or


$$\underline{\underline{-2V \leq v_o \leq 3V}}$$

Saturation

if $v_o < -2$ then
 $v_o = +10V$

if $v_o > 3V$ then
 $v_o = -15V$

Inductor

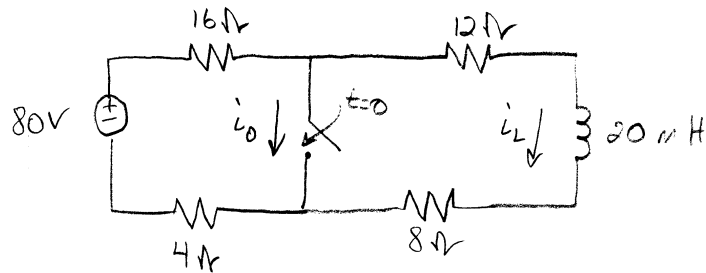

at $t < 0$ $v_L = 0$ since $\frac{di}{dt} = 0$

$$i_L(0^-) = \frac{80V}{(16+12+4+8)\Omega} = \frac{80V}{40\Omega} = \underline{2A}$$

at $t \rightarrow \infty$ "short out" the voltage source

thus $i_L = 0$


at $t = 0$ \rightarrow inductor cannot change abruptly

$$i_0(0^+) = \frac{80V}{16\Omega+4\Omega} - 2A = \frac{80V}{20\Omega} - 2A = 4A - 2A = \underline{2A}$$

at $t \rightarrow \infty$

$$i_0(\infty) = \underline{4A}$$

Capacitor

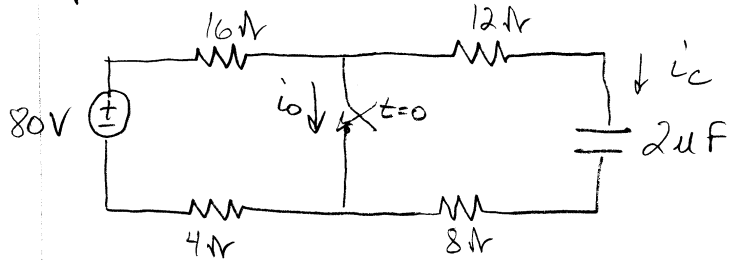

$$\text{at } t < 0 \quad u_c = 80V$$

$$i_c = 0A$$

$$\text{at } t \rightarrow \infty \quad u_c = 0V$$

$$i_c = 0A$$

at $t=0$ left loop + right loop


$$\text{left } i_{\text{left}} = \frac{80V}{20\Omega} = 4A$$

$$\text{Right } i_{\text{rt}} = \frac{80V}{20\Omega} = 4A$$

$$\text{total } i_o(t=0^+) = 4A + 4A = \underline{\underline{8A}}$$


Capacitors

C.A.P.

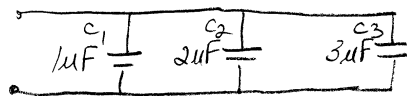

$$C_{ef} = C_1 + C_2 + C_3$$
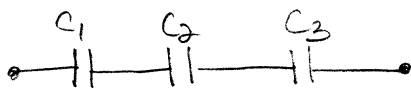
$$= 1 + 2 + 3 = \underline{\underline{6\mu F}}$$



$$\frac{1}{C_{ef}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{1\mu F} + \frac{1}{2\mu F} + \frac{1}{3\mu F}$$

$$= \frac{6+3+2}{6\mu F} = \frac{11}{6\mu F}$$

$$C_{ef} = \frac{6}{11} \mu F = \underline{\underline{0.55\mu F}}$$